

LM317 smooths but doesn't regulate

[Michael Dunn](#) - June 03, 2016

A well known power supply circuit is the capacitance multiplier. It doesn't regulate, but instead reduces ripple & noise while the output tracks at some fraction of the input voltage.

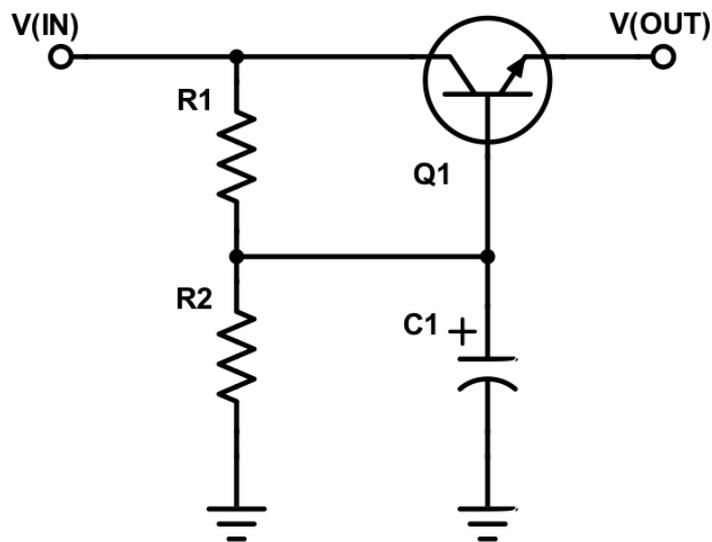


Figure 1 Standard "capacitance multiplier"

The R1/R2 voltage divider determines V_{OUT} (a V_{BE} below V_B), and must be chosen to account for the maximum ripple on the minimum V_{IN} .

If V_{IN} is regulated, the circuit can be used purely for low-level noise reduction. In this case, only one resistor is needed if you want to minimize the drop.


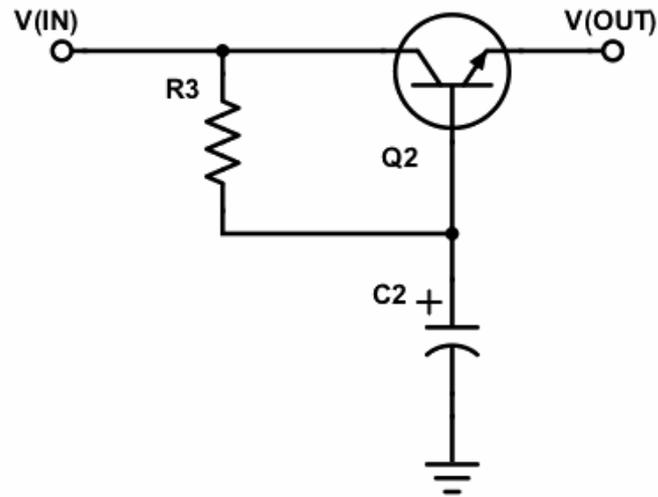


Figure 2 Minimal-drop multiplier reduces noise

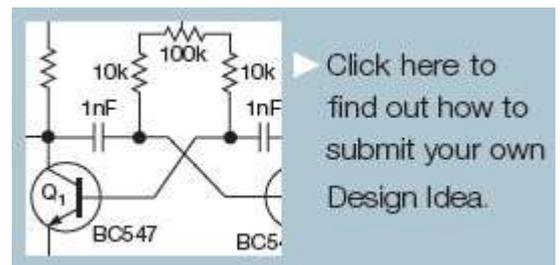The effect of the filter capacitor is said to be multiplied by the transistor's beta. With higher output currents though, this can lead to large capacitors, and more dissipation in the resistive divider than you might want, since sufficient base current must be supplied. Darlington transistors can help here, at the expense of a greater "dropout" voltage.



This Design Idea demonstrates an alternative approach to the capacitance multiplier (I expect it's been done before (perhaps even before I designed my version ca. 1983), but searching revealed no antecedents).

The circuit "reverses" the standard hookup of the [LM317](#) adjustable regulator. Normally, the ADJ pin connects to a voltage divider on V_{OUT} , and the LM317 regulates V_{OUT} by keeping it 1.25V above V_{ADJ} .

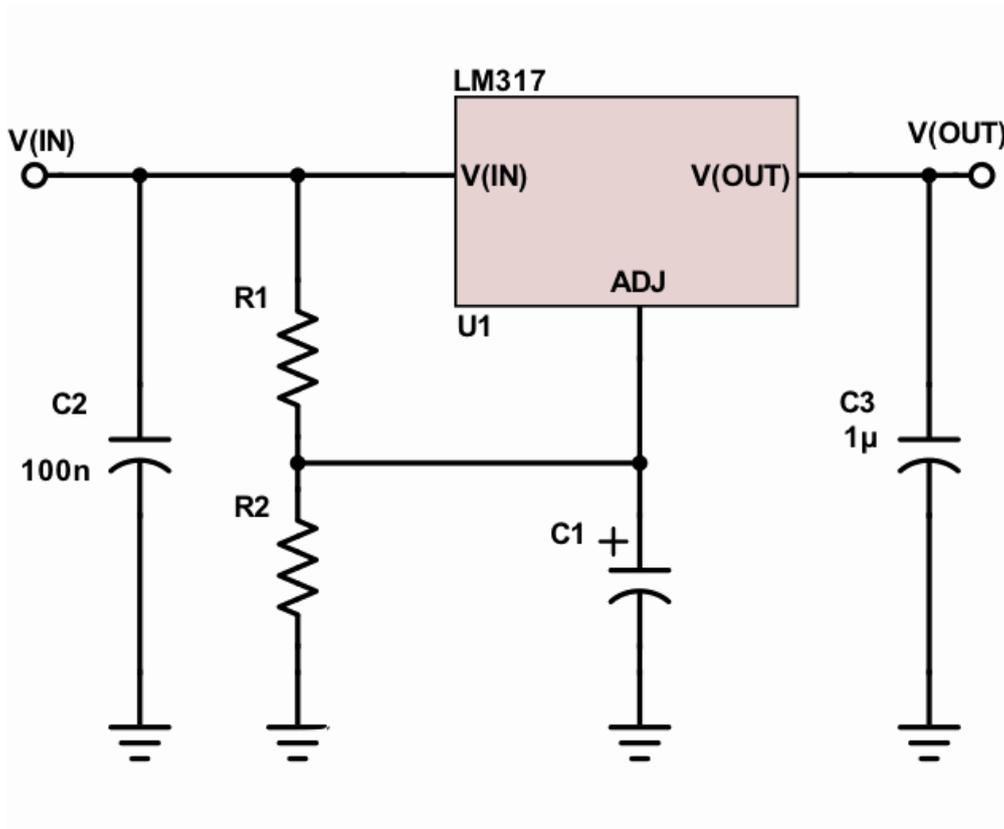


Figure 3 LM317-based capacitance multiplier

Here, V_{ADJ} is set to a filtered fraction of V_{IN} . V_{OUT} will be 1.25V above V_{ADJ} :

$$V_{OUT} = V_{IN} \cdot R2 / (R1 + R2) + 1.25V$$

If there's ripple/noise on V_{IN} , use the average voltage in the formula.

Note that the 317 has a 3V dropout voltage, so V_{OUT} must be lower than 3V below the lowest voltage on V_{IN} (including any ripple). Also keep in mind that V_{OUT} 's minimum load is 10mA; and that there can be up to 100μA of bias current through the ADJ pin (sourced from V_{IN}), so $R1 || R2$ shouldn't be too high.



Admittedly, there are better ways to accomplish the function described here, but I thought this worth sharing. Use as-is, or improve it to your liking.

I used this design back in the day to clean up a poorly regulated and noisy switcher output, at the same time, reducing the voltage. The supply fed a CRT display which had previously been plagued by visual grunge.

Also see:

- [Simple circuits reduce regulator noise floor](#)

- [Power Zener using the LM317](#)
- [Use an LM317 as 0 to 3V adjustable regulator](#)
- [Transistor boosts regulator current](#)

—[Michael Dunn](#) is an editor at EDN with several decades of electronic design experience in various areas.

Follow Michael Dunn at

