

solid state

Starter Kits Series: All-JFET MM/MC Phono Preamp, Part 2

By Erno Borbely

This flexible phono preamp design benefits from the author's 40 years of experience in the business.

The EB-804/419 is a high quality, low-cost all-JFET DC-coupled MM/MC phono preamp with on-board all-FET regulators. The combina-

tion of low input noise and high gain allows you to use it with practically all pickups on the market. The EB-804/419 uses a two-amplifier approach instead

of the usual single amplifier. This allows you to optimize it for low noise, RIAA accuracy, high gain, and dynamic range. The block schematic is shown in *Fig. 4*.

You can use the two-amp configuration in three different ways to realize the RIAA function: all active, all passive, or hybrid, meaning combination of passive and active. Two of these are supported in the EB-804/419: the hybrid and the all passive.

In *Fig. 4A* the amp on the left is a high-gain amplifier with extremely low input noise and flat frequency response. You can use it with 20 or 40dB gain by changing the feedback resistor. The R18/C11 network between the two amplifiers provides the 75 μ s passive rolloff. The second amp provides a further amplification of 24dB at 1kHz and at the same time boosts the bass according to the RIAA characteristics actively through R33/R32/R31/C14.

FIGURE 4: Block schematic for EB-804/419.


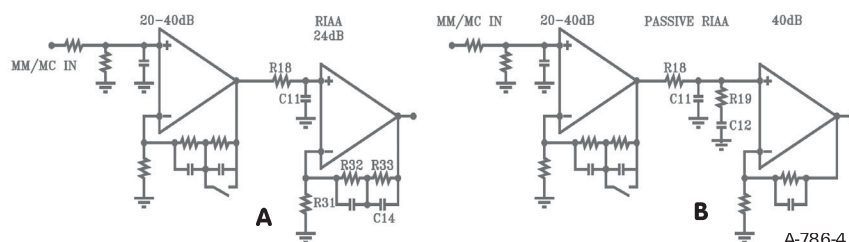


FIGURE 5: The EB-804/419 all-JFET MM/MC phono preamp.

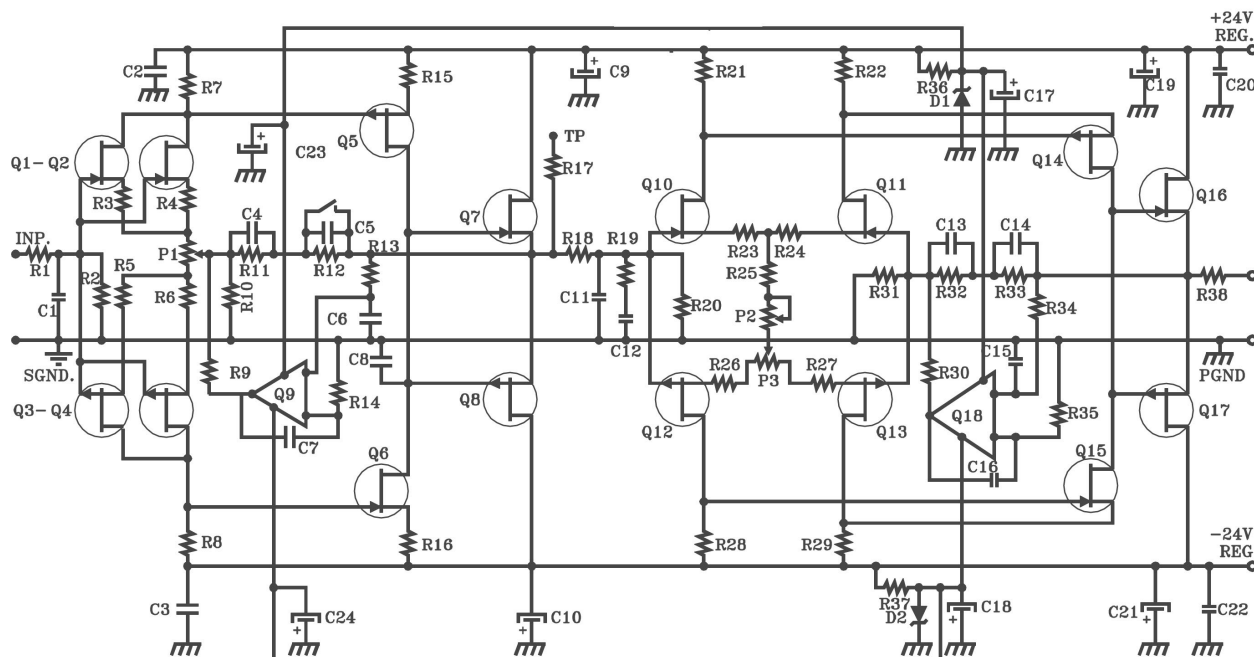

For those of you who want to experiment with all-passive equalization I have included the components for Walt Jung's network N2^{6.7} in *Fig. 4B*. Here both amplifiers provide flat frequency response and all RIAA equalization is done passively between the two amplifiers by R18/C11/R19/C12. MM gain is 44dB and MC gain is 64dB for the circuit in *Fig. 4A*. The gain in *Fig. 4B* depends on the all-passive equalization network discussed later. The Starter kit is supplied with components for the circuit in *Fig. 4A*. You can order

the all-passive network separately from Borbely Audio.

Figure 5 shows the schematic of the EB-804/419. The input stage is essentially the same as the one in *Fig. 3B*, but I have added source resistors to each of the input JFETs in case these are needed for matching and/or adjusting the drain current. Because the DC gain of the circuit can be very high (MC application and/or all-passive equalization), I use a servo circuit instead of capacitive coupling to keep the offset close to 0V.

I calculated the equivalent noise re-


sistance of the input stage using the drawing in *Fig. 6*. The JFETs are represented by the 55Ω equivalent noise resistors in series with the 10Ω source resistors. These are connected to P1, which is a 10Ω trimpot. Finally, the center point of the trimpot goes to R10 = 6R8 feedback resistor.

Because the JFETs are connected in parallel AC-wise, the equivalent noise resistance can be calculated to 25.5Ω. This will produce 92nV over the audio bandwidth. If you use this preamp with a 50Ω MC pickup, you will have a total noise of $\sqrt{128^2 + 92^2} = 157.6\text{nV}$, which results in a signal-to-noise ratio of 70dB referred to 0.5mV.

The 50Ω pickup itself contributes 128nV—i.e., if the amp were noiseless, the signal-to-noise ratio would be 71.8dB re 0.5mV. This means that the amp contributes only 1.8dB to the noise. You could decrease this by reducing/eliminating some of the noise-producing resistors in the input circuits.


If you select the input JFETs very closely, you could eliminate the 10Ω source resistors. The close matching could also eliminate the offset trimpot.

FIGURE 6: Calculating the equivalent noise resistance of the input stage.

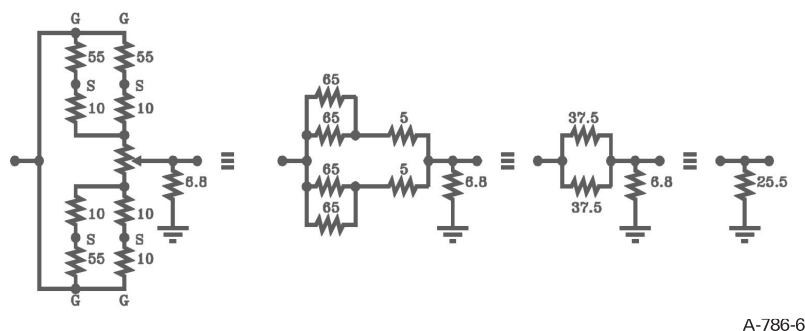

PRAXIS audio measurement system

- Provides full-featured customizable measurement including loudspeakers, room acoustics, noise surveys, transducers, electronics, vibration testing, PA alignment, and quality control.
- Flexible, portable system advances with the latest 24bit/192kHz soundcard converter technology.
- Latest version always available online.
- Informative website includes technical articles and downloadable demos.
- Friendly small company. No endless voicemail!

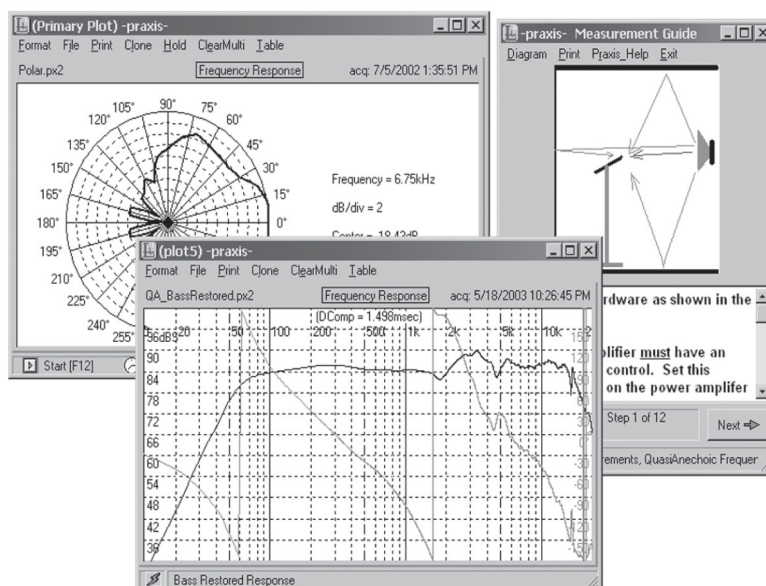

www.libinst.com

Liberty Instruments, Inc., P.O. Box 1454, West Chester, OH 45071 USA
Phone/Fax 513 755 0252, carolst@one.net

This would result in an equivalent noise resistance of 20.5Ω with a signal-to-noise ratio of 70.4dB, which means that the amp would contribute only about 0.4dB to the overall noise. For a 50Ω MC pickup this is probably the best you can achieve; however, for lower impedance/lower output MC pickups you will need to reduce the amp noise even further. (Calculate the signal-to-noise ratio for an MC pickup with 20Ω resistance!)

For MM the feedback resistor R10


is 75Ω, and the equivalent noise resistance is 93Ω. The equivalent short circuit input noise is 175nV. The total input noise with a 600Ω MM pickup is $\sqrt{(445^2 + 175^2)} = 478\text{nV}$, and the signal-to-noise ratio relative to 5mV is 80dB.

The second stage of the phono preamp uses the same topology as the Starter kit EB-604/410⁴. It provides the active bass boost of the RIAA characteristic through its feedback network. However, due to its high DC gain (in active eq.

mode the DC gain is 44dB!) a servo has been added. The servo amps are supplied with ±10V from shunt regulators.

The all-FET phono preamp is a very sensitive amplifier and is capable of picking up small signals not only through its inputs, but also through vibration. It is, therefore, very important to make the whole amp as “dead” as possible for vibration by using rubber stand-offs or mounting the whole board on a Teflon plate, 6-8mm thick. And a mumetal box will certainly put the icing on the cake.

FIGURE 7: EB-704/418 all-FET regulators.

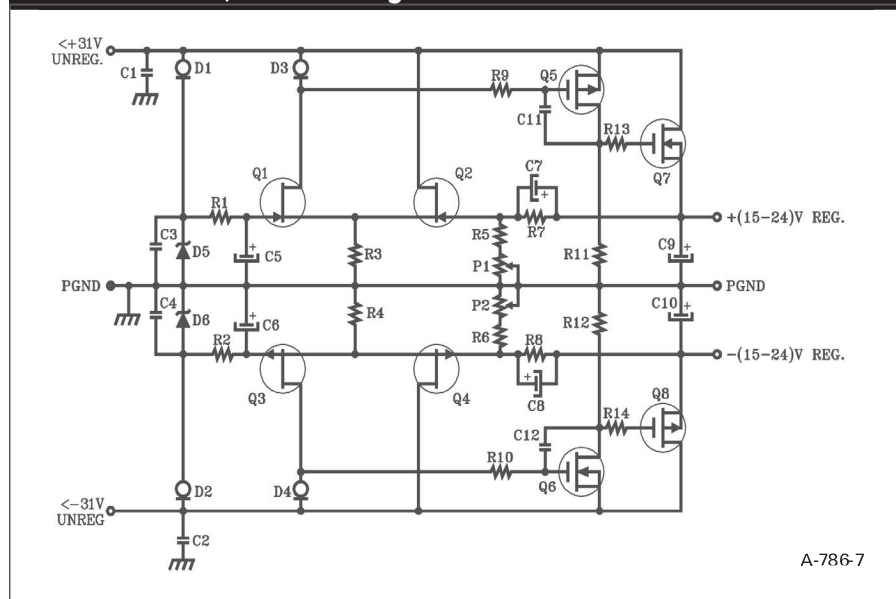

A-786-7


TYPICAL SPECIFICATIONS

Gain: 1st stage:	20 or 40dB
THD, 20dB gain, 3V/1kHz:	0.0033%
3V/10kHz:	0.005%
Gain: 2nd stage:	24dB
THD, 3V/1kHz:	0.003%
3V/10kHz:	0.007%
Max. output voltage:	approx. 9V RMS
Risetime	
(without RIAA network):	0.3/0.4μs
Freq. Response:	RIAA ±0.2dB
Equivalent input noise:	<100nV,
	20Hz-30kHz

THE EB-704/418 ALL-FET ON-BOARD REGULATOR

The schematic of the on-board EB-704/418 all-FET regulators is shown in Fig. 7. The topology is very similar to

FIGURE 8: Stuffing guide for MM/MC phono preamp EB-804/419 with EB-704/418 regulator.

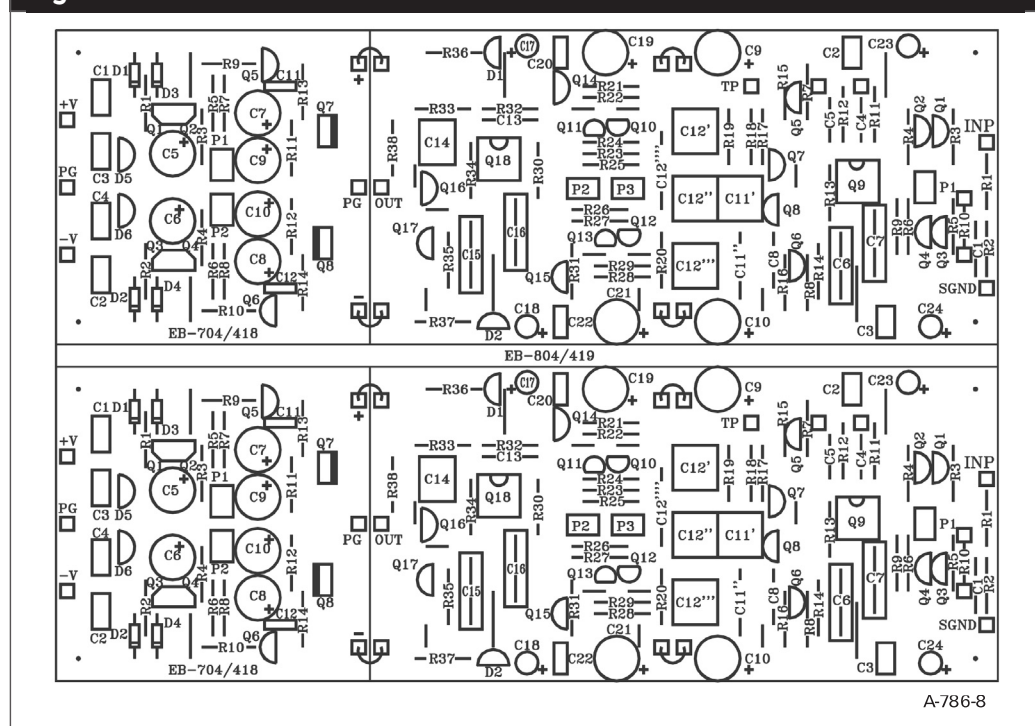

A-786-8

the EB-604/415 regulators used in the EB-604/410 line amp described in reference 4. However, I added Q7 and Q8 MOSFET source followers to be able to cope with the demand of the phono preamp (70mA). You can change output voltage between 15 and 25V with P1 and P2. If you use them with fixed 24V output, then you can short P1 and P2. Make R5 = R6 = 3k32.

Minimum input/output voltage differential is 3V, but 4V is recommended. Maximum unregulated input voltage is ±31V, and you must heatsink Q7/Q8. The output noise of the regulators is <5μV across the audio bandwidth. Recommended power supply is the EB-604/265. The stuffing guide for the EB-

804/419 phono preamp is shown in Fig. 8.

SETUP PROCEDURE

Start the assembly with the regulators, insert the solder pins and the jumpers, and then install the resistors, FETs, and finally the capacitors. Connect 332R/5W resistors between the +output and ground and the -output and ground of the regulators. Apply $\pm 29V$ unregulated DC to the regulators. Check the output voltage across the load resistors; it should be $24V, \pm 5\%$.

Next, begin the second stage of the


RIAA EQUALIZATION

The RIAA characteristic is defined by three time constants: $T_1 = 3180\mu s$, $T_2 = 318\mu s$, and $T_3 = 75\mu s$, corresponding to the crossover frequencies of 50, 500, and 2122Hz. A fourth time constant of $7950\mu s$ has been added by the IEC as an amendment to the RIAA characteristic; however, it has never been officially standardized by the RIAA. This time constant means a 6dB roll-off below 20Hz, and is meant to function as a rumble filter, reducing turntable/record related low-frequency disturbances. This feature is not included in the phono preamp described here.

The RIAA characteristic is shown in Fig. A with the asymptotes. It is specified in dB relative to 1kHz (0dB). It appears that the DC (or zero frequency) gain is 20dB (10 \times) higher than the gain at 1kHz. However, because of the interaction between the time constants, the actual DC gain is 9.898 \times the gain at 1kHz. This means that in an ideal RIAA preamp the 1kHz gain is always 0.101 \times DC gain (see reference 6: Walt Jung; *Op Amp Applications*, Chapter 6-1, Analog Devices, 2002, ISBN:0-916550-26-5), so specifying the gain at 1kHz also defines the gain for all other frequencies. ■

Accuracy, Stability, Repeatability

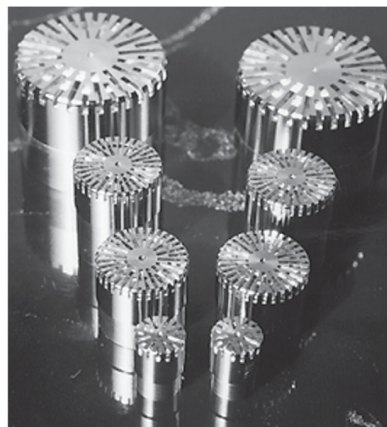Will your microphones be accurate tomorrow?



Next Week? Next Year? After baking them in the car???

ACO Pacific Microphones will!

Manufactured to meet IEC, ANSI and ASA standards.
Stainless and Titanium Diaphragms, Quartz insulators

Aged at 150°C.

Try that with a "calibrated" consumer electret mic!

ACO Pacific, Inc.

2604 Read Ave., Belmont, CA 94002

Tel: (650) 595-8588 FAX: (650) 591-2891 e-mail acopac@acopacific.com

ACOustics Begins With ACO™

FREE SAMPLE

IF YOU BUY,
SELL, OR COLLECT

OLD RADIOS, YOU NEED...



ANTIQUE RADIO CLASSIFIED

Antique Radio's Largest Monthly Magazine

100 Page Issues!

Classifieds - Ads for Parts & Services - Articles

Auction Prices - Meet & Flea Market Info. Also: Early TV, Art Deco,
Audio, Ham Equip., Books, Telegraph, 40's & 50's Radios & More...

Free 20-word ad each month for subscribers.

Subscriptions: \$19.95 for 6-month trial.

\$39.49 for 1 year (\$57.95 for 1st Class Mail).

Call or write for foreign rates.

Collector's Price Guide books by Bunis:

Antique Radios, 4th Ed. 8500 prices, 400 color photos \$18.95

Transistor Radios, 2nd Ed. 2900 prices, 375 color photos \$16.95

Payment required with order. Add \$3.00 per book order for shipping. In Mass. add 5% tax.



A.R.C., P.O. Box 802-A16, Carlisle, MA 01741

Phone: (978) 371-0512 — Fax: (978) 371-7129



Web: www.antiqueradio.com — E-mail: ARC@antiqueradio.com

phono preamp (R20 and onwards) by installing all solder pins, jumpers, resistors, JFETs, and capacitors. Put in the supply jumpers between the regulators and the second stage and short the input of the second stage (jumper across R20). Do not install Q18 just yet. Connect the $\pm 29\text{V}$ unregulated supply to the regulators. Measure the voltage drop across R22 (or R29) with a DVM and adjust it with P2 to 3V. Then check the offset voltage at the output and adjust it with P3 to 0V. Insert Q18 in the socket and recheck the offset; it should be less than a couple of mV after a few seconds.

Finally, assemble the input stage, except the RIAA components between the

two amps and Q9. Disconnect the supply jumpers between the regulators and the second stage and connect the regulators to the input stage with short wires. Short the +INP-pin of the input stage to SGND and check the voltage across R15 (or R16), which should be between 2.8V and 3.3V. Check the offset voltage of the input stage at the test-point TP and adjust it to zero with P1 (do this very carefully because the DC gain is very high). Install Q9 in the socket and recheck the offset, which should go down to a couple of mV in a few seconds.


Remove the jumper from R20, install the RIAA components, and connect the

proper supply jumpers between the regulators and the second stage and between the second stage and the input stage. Leave the short at the +INP and switch on the supply voltage. Check the offset at the output, which, after a couple of minutes, should be a few mV. A certain short-term drift of the offset is normal—remember, you are dealing with a total DC-gain of 84dB!

If you have audio measurement equipment, including an inverse RIAA circuit⁸ connect it to the input of the phono preamp and sweep the audio generator from 20Hz to 20kHz. Monitor the output of the phono preamp with an audio mV-meter. The output voltage should be constant with a maximum tolerance of $\pm 0.2\text{dB}$. If you have a scope, connect it to the output and make sure that the circuit does not overload during the measurement.

The phono preamp is now ready to be connected to your system. Changing between MM and MC means replacing R10. For MM, R10 = 75R and for MC it is 6R8. For MM, R2 is 47k, and for MC you will need to connect the appropriate load resistor at the input. You can solder this resistor either directly across the input terminals of the PCB or across the input connector on the back panel. A shunt capacitor (C1) might also be necessary; consult the datasheet of your pickup. **ax**

FIGURE A: The RIAA playback characteristic.

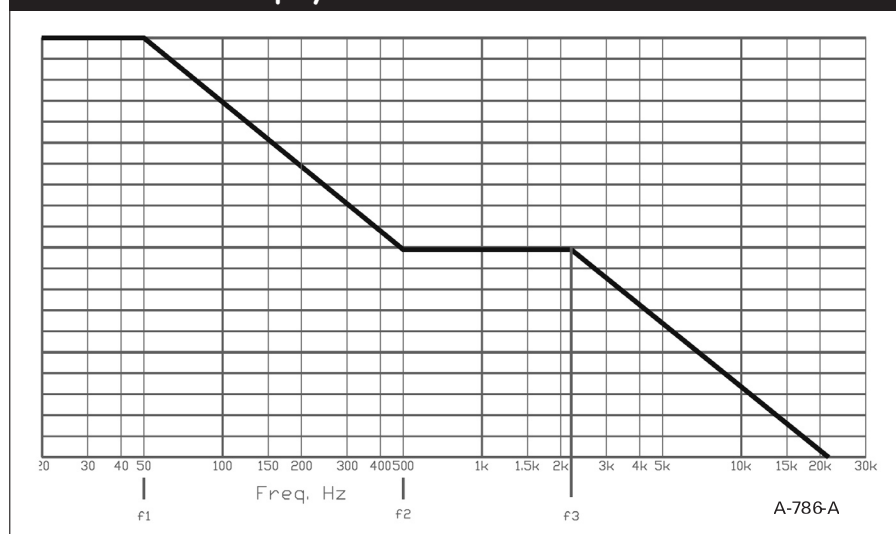

DESIGN PROCEDURE

The design procedure for the hybrid circuit in Fig. 4A is relatively simple:

1.) 75 μs passive network: choose an appropriate value for R18, which should be as low as possible because it influences the noise in the second stage, but high enough so that the input stage can drive it at high frequencies. If you use op amps for the two amps, the value should be between 600 Ω and several k Ω , depending on the drive capability of the op amps. I use R18 = 750 Ω for the discrete JFET input circuit used in the EB-804/419 because it is easy to make the 75 μs time constant with a C11 = 75 $\mu\text{s}/750 = 0.1\mu\text{F}$ capacitor. Because resistors are available with many more values than caps, you can also start

with the cap and calculate the necessary resistor. If you want to use a 47nF resistor, R18 = 75 $\mu\text{s}/47\text{nF} = 1.6\text{k}$. Naturally, you can also use two capacitors in parallel to make a convenient value.

2.) 318 and 3180 μ feedback network: choose a practical value for R33, which determines the 3180 μs time constant. Because I wanted to use the same cap as for the 75 μs , I calculated the resistor from R33 = 3180 $\mu\text{s}/0.1\mu\text{F} = 31\text{k}$ 8 (closest practical value is 31k6). Next calculate R31 from the formula that gives the DC (zero frequency) gain. The 1kHz gain is 0.101 \times DC gain, or the DC gain is 9.898 \times the 1kHz gain. I want a 1kHz gain of 24dB, which is 15.85 \times , so the DC gain will be 9.898 \times 15.85 = 156.88 \times . R1 = (9.898 \times R3)/(9 \times DC gain) = 222 Ω (closest value is 221R). Finally, calculate R2 from (R3/9)-R1 = 3290

(closest value: 3k32).

For the all-passive equalization in Fig. 4B I used Walt Jung's network N2⁷ with the following component values:

Theoretical:	Closest fit:
R18 = 7k29	7k32
R19 = 1k06	1k05
C11 = 0.3 μF	0.3 μF
C12 = 0.1029 μF	0.1 μF + 3nF

All network components should be precision ones: resistors 1% or better and caps 2% or better. The Starter kit EB-804/419 is delivered with 0.1% Dale CMF-55-143 non-magnetic resistors and 1 and 2% polypropylene and polystyrene capacitors. Using Walt's inverse RIAA network⁸ both networks show better than $\pm 0.2\text{dB}$ accuracy across the audio range. ■

Acknowledgements

Many thanks to Walt Jung for letting me use his passive RIAA network in the phono preamp and for his valuable comments and suggestions regarding this article.

The Starter Kits EB-804/419 and EB-704/418 (available from Borbely Audio, Angerstr. 9, 86836 Obermeitingen, Germany, +49/8232/903616, sales@borberlyaudio.com) are the intellectual property of Erno Borbely/Borbely Audio. Commercial use or duplication in any form is not authorized without a license agreement.

REFERENCES

4. Erno Borbely, "Starter Kits, Part I: EB-604/410 All-JFET Line Amp," audioXpress, March 2005, p. 9.
5. Erno Borbely, "The All-JFET Line Amp" audioXpress, May 2002, p. 28.
6. Walt Jung, Op Amp Applications, Chapter 6-1, Analog Devices, 2002, ISBN 0-916550-26-5.
7. Walt Jung, "Topology Considerations for RIAA Phono Preamplifiers," AES Preprint 1719, 67th Convention, 1980 Oct. 31/Nov. 3 New York. (http://home.comcast.net/~walt-jung/wsb/PDFs/Topology_Considerations_for_RIAA_Phono_Preamps.pdf)
8. Walt Jung and Stanley Lipshitz, "A High Accuracy Inverse RIAA Network," The Audio Amateur, 1/80, p. 22.

PARTS LIST

PHONO PREAMP EB-804/419

Resistors, Trimpots

R1	Short for MC 10R for MM
R2	47k5 for MM See spec for MC
R3, R4, R5, R6	10R
R7, R8, R11	681R
R9	2K21
R10	6R8 for MC 75R for MM
R12	Optional for passive eq.
R13, R14, R20, R34, R35	1M
R15, R16, R22, R29	332R
R17, R25, R38	47R5
R18	750R
R19	See passive eq.
R21, R28	1k5
R23, R24	100R
R26, R27	75R
R30	100k
R31	221R
R32	3k32
R33	31k6
R36, R37	1k2
P1	10R COPAL
P2	200R COPAL
P3	50R COPAL

Capacitors

C1, C8	100pF, 160V, PS
C2, C3, C20, C22	0.1µF, 100V, PP
C4, C13	33pF, 160V, PS
C5	Appl. Dependent
C6, C7, C15, C16	0.22µF, 250V, PP
C9, C10, C19, C21	47µF, 35V
C11, C14	0.1µF, 100V, 1%, ERO PP
C12	See passive eq.
C17, C18, C23, C24	100µF, 25V, ROE EKO

FETs, Diodes

Q1, Q2	K170GR (Idss: 3.5-4mA)
Q3, Q4	J74GR (Idss: 3.5-4mA)
Q5, Q14	J74V (Idss: >10mA)

Q6, Q15	K170V (Idss: >10mA)
Q7, Q16	K170BL (Idss: 8-10mA)
Q8, Q17	J74 (Idss: 8-10mA)
Q10, Q11	K170BL/V*
Q12, Q13	J74BL/V**
Q9, Q18	LF411CN
D1, D2	LM4040DIZ-10

* Dual JFET K389BL/V can be used for Q10-Q11

** Dual JFET J109BL/V can be used for Q12-Q13

Miscellaneous

40 × 1mm solder pins

PCB: EB-804/419

REGULATORS EB-704/418

Resistors, Trimpots

R1, R2, R5, R6	3K09
R3, R4	1K82
R7, R8	8K25
R9, R10, R13, R14	100R
R11, R12	10K
P1, P2	5K COPAL

Capacitors

C1, C2, C3, C4	0.1µF, 100V, PP
C5, C6	220µF, 16V
C7, C8, C9, C10	47µF, 35V
C11, C12	33pF, 400V, MICA


FETs, Diodes

Q1, Q2	K170BL/V* (Matched, Idss: >9mA)
Q3, Q4	J74BL/V** (Matched, Idss: >9mA)
Q5	J148
Q6	K982
Q7	K2013
Q8	J313
D1, D2	E202 (2mA)
D3, D4	E102 (1mA)
D5, D6	LM329DZ (6.9V ref.)

* Dual JFET K389BL/V can be used for Q1-Q2

** Dual JFET J109BL/V can be used for Q3-Q4

Toroids for Audio

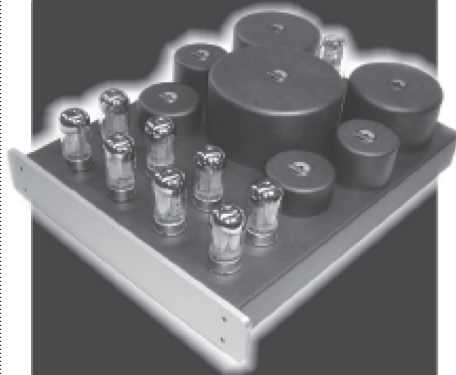

Tube Output

Toroidal transformers for tube output applications.

Electrostatic

Step-up toroidal transformers.

Solid State Power

Low noise, low inrush 500 to 2000VA.

Standard Power

Designed for general purpose applications. From 15 to 1500VA.



Part No. **7398-B2-00**
 Application **Solid-State Amp**
 Primary **115/230VAC**
 Power **2000VA**
 Secondary **either 4 x 45VA 11A
 or 2 x 90CT 11A
 or 90CT 22A
 or 180CT 11A**
 Case **Aluminum**
 Finish **Textured black**
 Size **250 x 150mm**



PLITRON
 MANUFACTURING INC
 8-601 Magnetic Drive
 Toronto, ON M3J 3J2
 Canada
 416-667-9914
 FAX 667-8928
1-800-PLITRON (754-8766)
www.plitron.com

www.plitron.com