

DESIGN IDEAS

the count is 00 at power-up. You decode the outputs of the counter with a 2-to-4 line decoder (IC₄) to select one of the output lines, $\bar{0}$ through $\bar{3}$. The outputs of the decoder provide wave drive or 2-phase drive.

Wave drive has one phase on at any given time, and the phases are energized sequentially. **Fig 2a** shows the state table for wave drive. The outputs of the decoder are inverted to turn on the power amplifiers for each phase.

In 2-phase drive, two phases are on at any given instant. The state table for 2-phase drive is shown in **Fig 2b**. To derive the driving sequence for this mode, the outputs are combined two at a time as inputs to the exclusive-OR gates. The gate outputs are connected to the power-amplifier inputs. The power amplifier for one phase is shown in **Fig 3**.

EDN

To Vote For This Design, Circle No 749

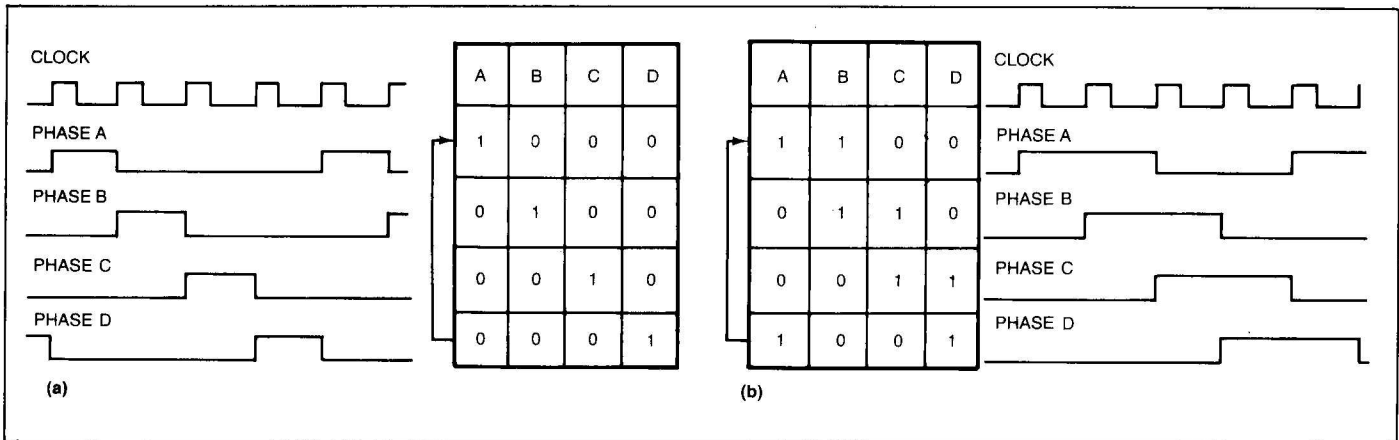


Fig 2—State tables and drive waveforms depict simple control schemes for 1-phase (a) and 2-phase (b) stepper motors.

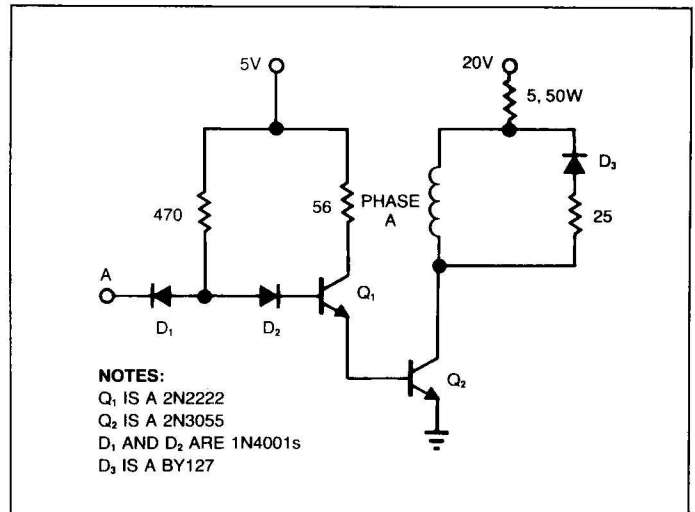


Fig 3—You'll need one of these power amplifiers for each phase of your stepper motor. Choose Q₂ to reflect the drive requirements of your motor.

Enhanced op amp delivers 100V p-p

Barry Kline
 Technicare Corp, Solon, OH

If you need an amplifier that provides more than $\pm 50V$ output swing along with the high gain and low offset of a high-performance op amp, consider the **Fig 1** circuit. It employs a gain stage (Q₁-Q₄, R₁-R₄) to multiply the op amp's $\pm 10V$ output swing to the desired level. The combined op amp and gain stage may be regarded as a high-voltage amplifier.

The gain stage is based on a design by Jerald Graeme (**Ref 1**), but adds current feedback via R₄ to achieve three performance improvements: reduction of open-loop output impedance (reduced sensitivity to changes

in load current); reduction of output current I_A from the op amp; and increased dynamic range due to a reduction in signal voltage across the current-sensing resistors R_{1A} and R_{1B}.

Q₁ and Q₃ act as cascode stages for the op-amp supply currents I_{A1} and I_{A2}. Q₂ and Q₄ sense these currents and provide amplified output currents I₁ and I₂:

$$I_{O1} = I_{A1} \times \frac{R_1}{R_2}$$

$$I_{O2} = I_{A2} \times \frac{R_1}{R_2} \quad (1)$$

Also, because the difference in supply currents is equal to the op-amp output current (I_A = I_{A1} - I_{A2}),

DESIGN IDEAS

$$I_{01} - I_{02} = (I_{A1} - I_{A2}) \times \frac{R_1}{R_2} = I_A \times \frac{R_1}{R_2}. \quad (2)$$

Feeding this current imbalance back to the op-amp output terminal provides negative feedback for the booster stage. Recall that:

$$I_{O1} - I_{O2} = I_A \times \frac{R_1}{R_2}. \quad (3)$$

In addition,

$$I_4 = (I_{A1} - I_{A2}) - I_L = \left(I_A \times \frac{R_1}{R_2} \right) - I_L.$$

But, $I_A = I_3 - I_4$.

$$\text{So, } I_4 = (I_3 - I_4) \times \left(\frac{R_1}{R_2} \right) - I_L. \quad (4)$$

$$\text{Or, } I_4 \left(1 + \frac{R_1}{R_2} \right) = \left(I_3 \times \frac{R_1}{R_2} \right) - I_L .$$

Substitute V_A for the op amp's output voltage:

$$\begin{aligned} I_4 &= \frac{V_{OUT} - V_A}{R_4} \\ I_3 &= \frac{V_A}{R_3} \\ I_L &= \frac{V_{OUT}}{R_L}. \end{aligned} \quad (5)$$

Therefore:

$$\frac{V_{OUT} - V_A}{R_4} \left(1 + \frac{R_1}{R_2} \right) = \frac{V_A R_1}{R_3 R_2} - \frac{V_{OUT}}{R_L}. \quad (6)$$

The equation can be solved for voltage gain of the booster stage:

$$\frac{V_{\text{OUT}}}{V_A} = \frac{1 + \frac{R_4}{R_3} \left(\frac{R_1}{R_1 + R_2} \right)}{1 + \frac{R_4}{R_3} \left(\frac{R_2}{R_1 + R_2} \right)} \quad (7)$$

$$= 1 + \frac{R_4}{R_3} \left(\frac{R_1}{R_1 + R_2} \right) \left(\frac{R_L}{R_0 + R_1} \right).$$

Output impedance (R_o) is:

$$R_0 = \frac{R_4 \times R_2}{R_1 + R_2}. \quad (8)$$

To calculate the op amp's output current (I_A):

$$\begin{aligned} I_A &= I_3 - I_4 = \frac{V_A}{R_3} - \frac{V_{OUT} - V_A}{R_4} \\ &= V_A \left(\frac{1}{R_3} + \frac{1}{R_4} - \frac{V_{OUT}}{V_A R_4} \right). \end{aligned} \quad (9)$$

The no-load booster gain is obtained by setting R_L to infinity in **Eq 7**:

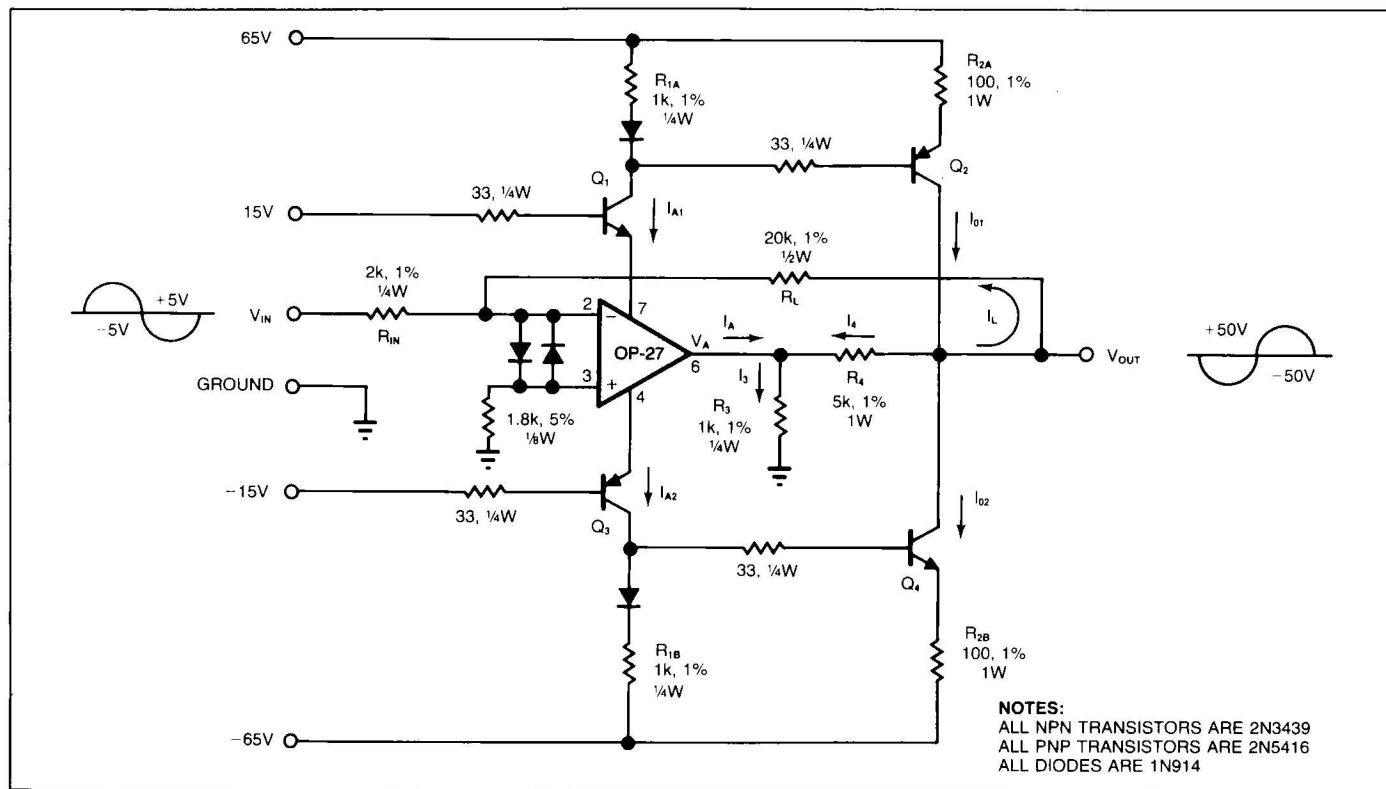


Fig 1—Gain stage with current feedback boosts a conventional op amp's output to more than 100V p-p.

Design Entry Blank

\$75 Cash Award for all entries selected by editors. **An additional \$100 Cash Award** for winning design each issue, determined by vote of readers. **Additional \$1500 Cash Award** for annual Grand Prize Design, selected among biweekly winners by vote of editors.

To: Design Ideas Editor
EDN
Cahners Publishing Co
275 Washington St, Newton, MA 02158

I hereby submit my entry for
EDN's Design Ideas program.

Name _____

Title _____ Phone _____

Company _____

Division (if any) _____

Street _____

City _____ State _____ Zip _____

Design Title _____

Home Address _____

Social Security No _____

Entry blank must accompany all entries. Design entered must be submitted exclusively to EDN, must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed _____

Date _____

Your vote determines this issue's winner. All designs published win \$75 cash. All issue winners receive an additional \$100 and become eligible for the annual \$1500 Grand Prize.

Vote now, by circling the appropriate number on the reader inquiry card.

Submit your own design, too. Mail entries to Design Ideas Editor, EDN, 275 Washington St, Newton, MA 02158.

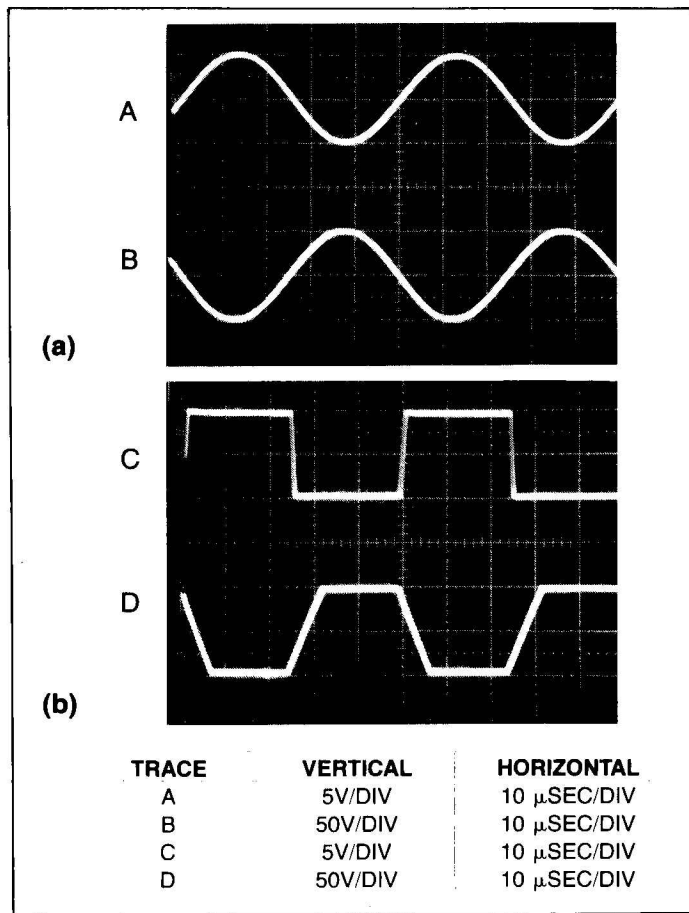


Fig 2—The Fig 1 circuit produces 100V p-p sine- and square-wave outputs—a and b, respectively. Slew response to the square wave is a product of the OP-27 slew rate (2.8V/μsec typ) and gain of the booster stage (approximately 5.5).

$$\frac{V_{OUT}}{V_A} = 1 + \frac{R_4}{R_3} \left(\frac{R_1}{R_1 + R_2} \right) \quad (10)$$

Substituting the **Eq 10** no-load booster gain into **Eq 9** yields:

$$I_A = \frac{V_A}{R_3} \left(\frac{R_2}{R_1 + R_2} \right) \quad (11)$$

The use of current feedback reduces the output impedance and the required op-amp output current by a factor of $R_2/(R_1 + R_2)$. Also, reducing I_A reduces signal current variations in the supply lines.


Be careful not to exceed the power-dissipation capacity of components Q_2 , Q_4 , R_2 , R_4 , and R_L . In addition, quiescent current in Q_2 and Q_4 is proportional to the current gain R_1/R_2 , so choose this ratio carefully. **EDN**

Reference

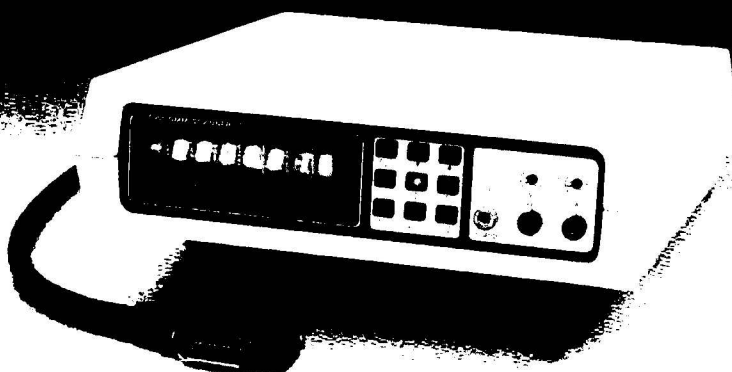1. Graeme, Jerald G, *Designing with Operational Amplifiers—Applications Alternatives*, McGraw-Hill, 1977, pg 14.

To Vote For This Design, Circle No 750

READING THIS AD CAN SAVE YOU \$500 OR MORE—AND GIVE YOU BETTER PERFORMANCE IN THE BARGAIN.



Introducing PREMA High Performance 6-1/2 Digit Multimeters

We're PREMA, and we're internationally renowned for top performance digital multimeters. We're now in the U.S., and we'd like you to take a look at how we stack up against the "major manufacturers" you already know about. Here's a brief feature and cost comparison between a few of the more popular 6-1/2 digit units.

MFG Model	Digits	Prg	IEEE	Vdc	Vac	DC Amp	AC Amp	Published 1-Piece Price
Prema 5000	6-1/2	✓	✓	✓	✓	✓	✓	\$1600
Fluke 8505A	6-1/2	No	Option	✓	✓	Option	Option	\$3195
Kelthly 193	6-1/2	✓	✓	✓	✓	Option	Option	\$2100
HP 3456A	6-1/2	SM*	✓	✓	✓	No	No	\$3745
Solartron 7060 C	6-1/2	No	✓	✓	✓	✓	✓	\$2695

In addition, PREMA's Model 5000 features a resolution of 100 nV, 1 GΩ input resistance up to ± 2V, continuous averaging, automatic zero control, integration time from 100 ms to 10 sec., and a state-of-the-art, 4 pole 10 or 20 channel scanner option.

Price a PREMA For more complete comparison and technical information on our 6-1/2 digit units, give us a call today. Once you know the facts we think you'll agree that a PREMA is simply the best buy possible. PREMA PRECISION ELECTRONICS, 6290 Sunset Blvd., Los Angeles, CA 90028. Phone: (213) 463-2294

*Storage Memory



See us at Wescon Booth 5613

CIRCLE NO 205

DID YOU KNOW

EDN has the largest circulation of any
electronic industry publication in the world
— 129,518 qualified subscribers.

EDN

SIGNALS & NOISE

was mandated by the government because (statistically) it helps to reduce the number of rear-end collisions.

Yes, I am all for the use of modern technology and mathematics to build safer, more efficient, and more reliable cars. Mr Bismarck should open his closed mind and take another look at this technology.

Sincerely,

N Paul Galluzzi, EE

Dynamics Research Corp

Wilmington, MA

Corrections

Please note the following corrections to two equations in the Design Idea "Enhanced op amp delivers 100V p-p" by Barry Kline (EDN, September 5, pg 309). Eq 4 on pg 311 should read:

$$I_4 = (I_{O1} - I_{O2}) - I_L$$

$$= \left(I_A \times \frac{R_1}{R_2} \right) - I_L$$

Eq 7 should read:

$$\frac{V_{OUT}}{V_A} = \frac{1 + \frac{R_4}{R_3} \left(\frac{R_1}{R_1 + R_2} \right)}{1 + \frac{R_4}{R_L} \left(\frac{R_2}{R_1 + R_2} \right)}$$

$$= \left[1 + \frac{R_4}{R_3} \left(\frac{R_1}{R_1 + R_2} \right) \right] \left(\frac{R_L}{R_O + R_L} \right)$$

In addition, in the Design Idea "Detect out-of-bound pulse widths" by Dil Sukh Jain (EDN, September 19, pg 242), the statement "Each NAND-gate output is high unless either or both inputs are low" is incorrect. The statement should read: "Each NAND-gate output is high when either or both inputs are low." Also, in IC_{1b} in Fig 1, Q₂ should be Q₂.

Finally, in the Design Idea entitled "Switch lets you select memory devices" (EDN, July 25, pg 312), the authors' names appeared in reverse order. The article was contributed by D V Poorniah and M O Ahmad, in that order.