

PHASE CHECK FOR AUDIO SYSTEMS



While setting up and connecting audio equipment it is important to have all the units — microphone, loudspeakers and everything in between — ‘in phase’, that is, interconnected with the right polarity. The low-cost instrument described here is particularly handy for checking out the phase of almost any audio system, whether installed in a living room, in a car, in a studio, or on a stage.

K. Orlowski

REVERSED phase connections in an audio equipment system give strange and unpredictable effects such as the unwanted attenuation or boosting of a particular frequency range, jet-plane effects, whistling noises, or amplifier output power which does not seem to produce any usable sound level. To avoid these problems, use the simple instrument described here. Based on a transmitter and a receiver with a simple good/fault indication, the instrument will check out the system from the input (microphone or line input) right through to the output (loudspeaker or line output).

The transmitter supplies positive or negative needle pulses, which are fed either electrically to an equipment input, via the line-cinch output socket, or acoustically to a microphone, via the built-in loudspeaker. Accordingly, the receiver has an electrical (line) input and an acoustic (microphone) input.

The drawings in Fig. 1 illustrate two ways of using the transmitter and the receiver for phase tests on audio equipment.

Figure 1a shows the set-up used to check the polarity of a microphone, and Fig. 1b that used to ensure a loudspeaker is connected

the right way around. The LEDs on the receiver provide a quick indication whether or not the received pulses have the same polar-

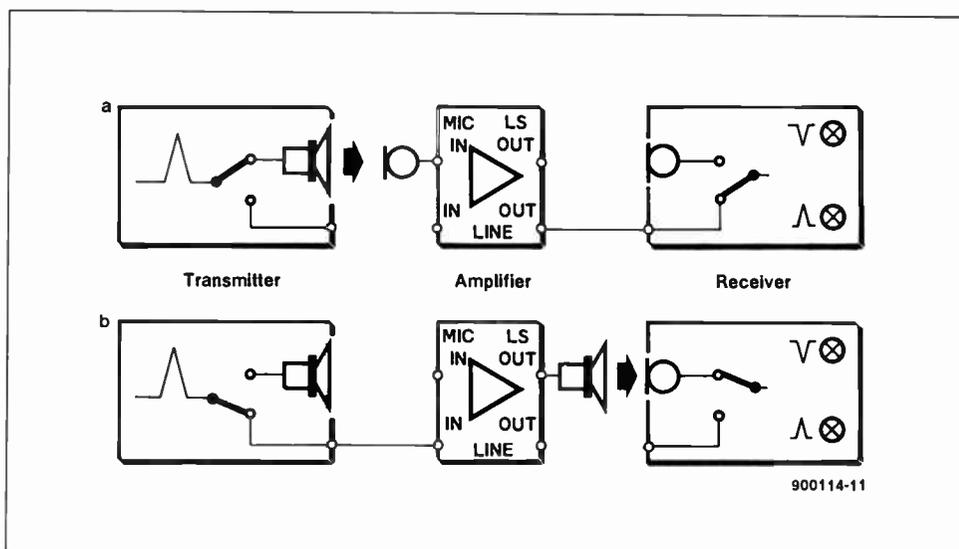


Fig. 1. Application examples of the phase-check system.

ity as the transmitted pulses. If the receiver indicates the opposite polarity of the transmitter, the chances are pretty high that there is a reversed signal connection somewhere in the system.

The pulse transmitter

The needle pulses are generated by oscillator IC1a (see Fig. 2), which is built from a NAND gate with two Schmitt-trigger inputs. After applying the supply voltage, these inputs take on complementary logic levels, i.e., one is high, the other is low. Consequently, the output of the gate is logic high. Capacitor C2 is charged via resistor R1, until the voltage on it reaches the high threshold voltage of about 5.5 V. Next, the output of the Schmitt-trigger toggles to 0, so that C2 is discharged via D1 and R2, until the low threshold voltage of about 3 V is reached. The NAND gate toggles, and the charging of C2 starts again.

The above process is cyclical and results in a self-oscillating circuit. Since R2 is much smaller than R1, the discharge time of C2 is much shorter than the charge time. As a result, the on-off (mark-space) ratio of the output signal is about 2 ms/1 s, or 0.002. Mind you, 'off' means 'logic high' here since we are dealing with a NAND gate.

The oscillator output signal is fed to two sub-circuits. One is a small loudspeaker driver based on emitter follower T2. The loudspeaker connections can be swapped by switch contacts S1c and S1d. When an oscilloscope is connected to the loudspeaker, it indicates negative-going needle pulses with the switch set to the centre position, and positive-going pulses with the switch set to the upper position. Likewise, in the other signal branch, the polarity is changed by switching transistor T1 from a common-emitter circuit (S1b at centre position) to a common-collector circuit (S1b at centre position). Coupling capacitor C3 takes the test signal to an attenuator that supplies output levels of 1 Vpp (0 dBV), -20 dBV and -40 dBV.

The receiver

The circuit diagram of the receiver (Fig. 3) shows that two almost identical detectors are used. The test signal is supplied to the two voltage amplifiers T1-T2 and T4-T5 either by the electret microphone, or by the signal source connected to K1. In the latter case, the signal is taken through a high-pass filter, R1-C3, before it arrives at a voltage limiter, D1-D2. The input source, microphone or line, is selected with switch S1. The voltage amplifiers are complementary circuits: T1-T2 amplifies the negative pulses, T4-T5 the positive pulses.

The two monostables in IC1 have different networks at their trigger inputs to enable them to respond to negative pulse edges (IC1a) or positive pulse edges (IC1b). To prevent the trailing edge of a pulse triggering the wrong monostable, IC1a and IC1b disable one another when one of them is actuated. The monostables thus allow the circuit to determine whether a pulse starts with a

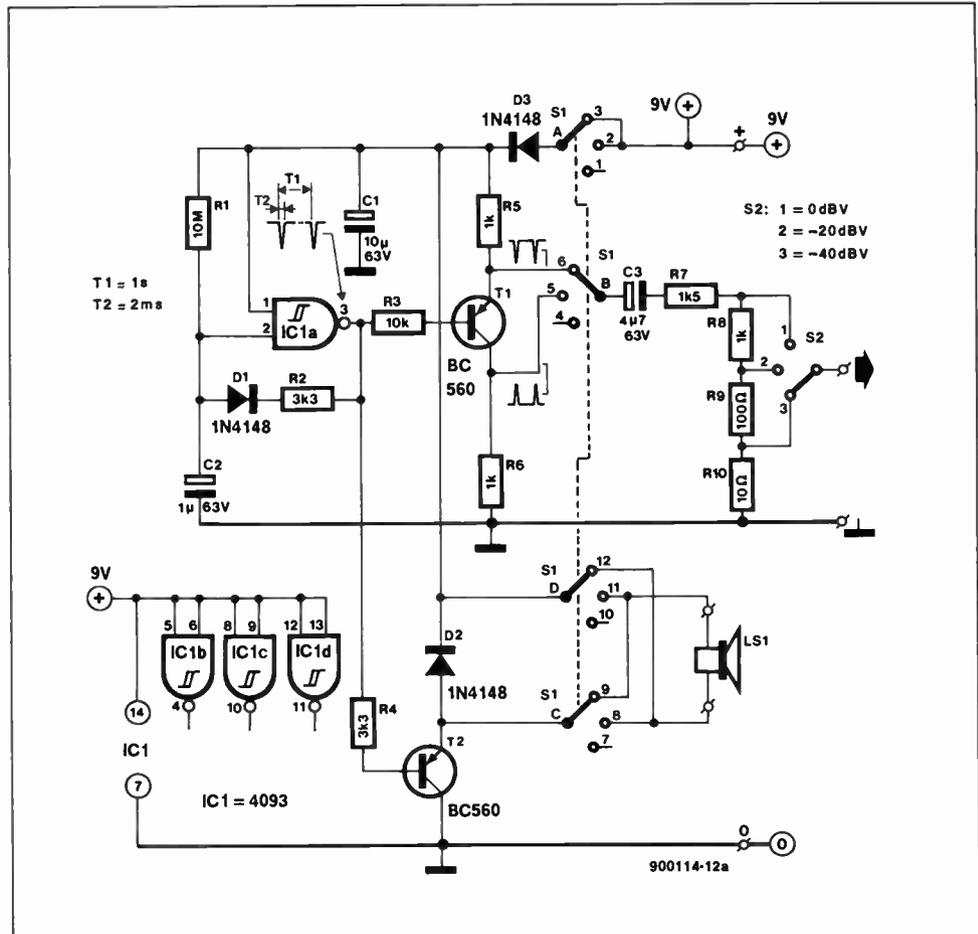


Fig. 2. Circuit diagram of the pulse transmitter.

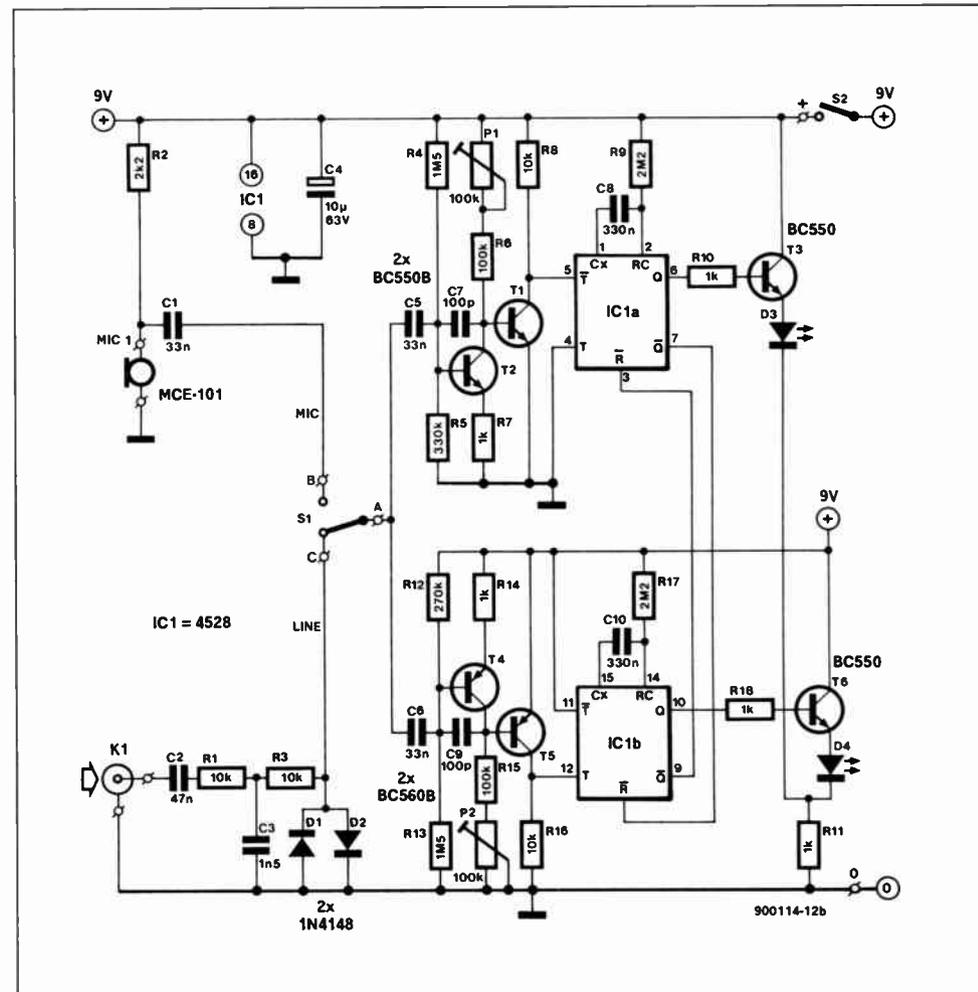


Fig. 3. Circuit diagram of the pulse receiver. The polarity of the measured signal is indicated by two LEDs, D3 and D4.

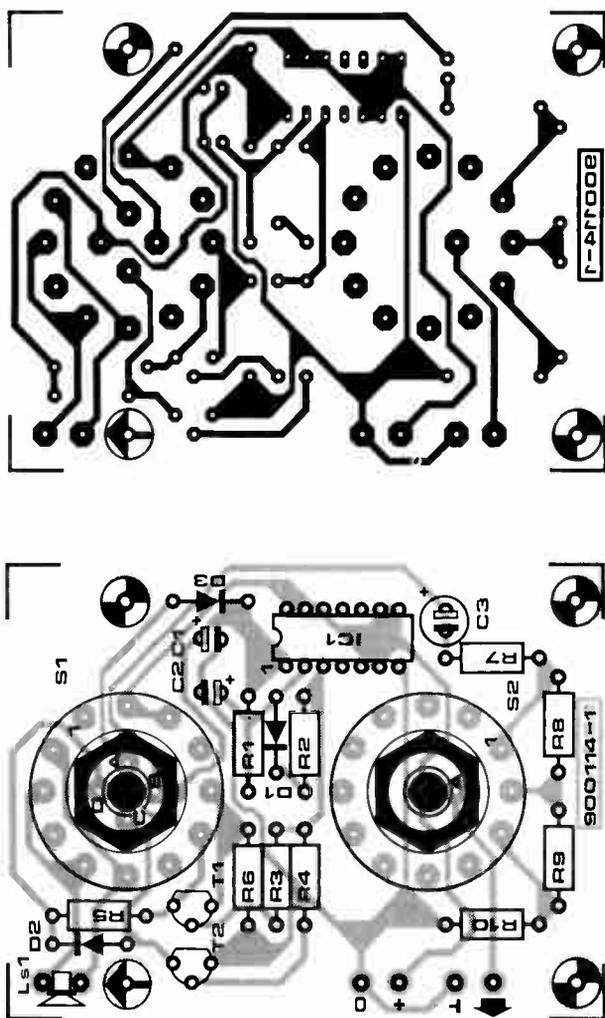


Fig. 4a. Single-sided printed circuit board for the pulse transmitter.

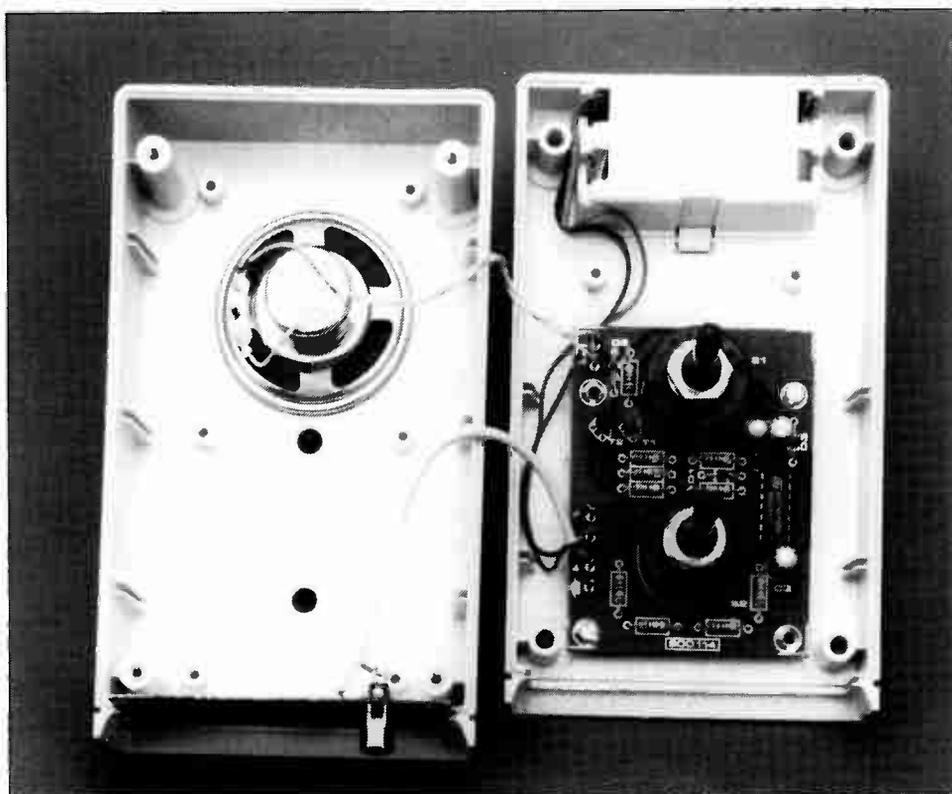


Fig. 5. A look inside the completed pulse transmitter.

COMPONENTS LIST

TRANSMITTER:

Resistors:

- | | | |
|---|---------------|----------|
| 1 | 10M Ω | R1 |
| 2 | 3k Ω 3 | R2;R4 |
| 1 | 10k Ω | R3 |
| 3 | 1k Ω | R5;R6;R8 |
| 1 | 1k Ω 5 | R7 |
| 1 | 100 Ω | R9 |
| 1 | 10 Ω | R10 |

Capacitors:

- | | | |
|---|-----------------------|----|
| 1 | 10 μ F 63V radial | C1 |
| 1 | 1 μ F 63V radial | C2 |
| 1 | 4 μ F7 63V radial | C3 |

Semiconductors:

- | | | |
|---|--------|----------|
| 3 | 1N4148 | D1;D2;D3 |
| 2 | BC560 | T1;T2 |
| 1 | 4093 | IC1 |

Miscellaneous:

- | | | |
|---|--|-----|
| 1 | 3-way 4-pole rotary switch for PCB mounting | S1 |
| 1 | 12-way 1-pole rotary switch for PCB mounting | S2 |
| 1 | 8- Ω loudspeaker, dia. 50 mm | LS1 |
| 1 | ABS enclosure, e.g., OKW A9409126 | |
| 1 | clip for 9-V battery | |
| 1 | phono socket | |
| 1 | printed-circuit board 900114-1 | |

RECEIVER:

Resistors:

- | | | |
|---|------------------------|--------------------|
| 4 | 10k Ω | R1;R3;R8;R16 |
| 1 | 2k Ω 2 | R2 |
| 2 | 1M Ω 5 | R4;R13 |
| 1 | 330k Ω | R5 |
| 2 | 100k Ω | R6;R15 |
| 5 | 1k Ω | R7;R10;R11;R14;R18 |
| 2 | 2M Ω 2 | R9;R17 |
| 1 | 270k Ω | R12 |
| 2 | 100k Ω preset H | P1;P2 |

Capacitors:

- | | | |
|---|-----------------------|----------|
| 3 | 33nF | C1;C5;C6 |
| 1 | 47nF | C2 |
| 1 | 1nF5 | C3 |
| 1 | 10 μ F 63V radial | C4 |
| 2 | 100pF | C7;C9 |
| 2 | 330nF | C8;C10 |

Semiconductors:

- | | | |
|---|-----------|-------------|
| 2 | 1N4148 | D1;D2 |
| 1 | red LED | D3 |
| 1 | green LED | D4 |
| 4 | BC550B | T1;T2;T3;T6 |
| 2 | BC560B | T4;T5 |
| 1 | 4528 | IC1 |

Miscellaneous:

- | | | |
|---|-----------------------------------|------|
| 1 | electret microphone | Mic1 |
| 1 | phono socket | K1 |
| 1 | miniature SPDT switch | S1 |
| 1 | miniature SPST switch | S2 |
| 1 | clip for 9V PP3 battery | |
| 1 | ABS enclosure, e.g., OKW A9409126 | |
| 1 | printed-circuit board 900114-2 | |

