

DESIGN IDEAS

IC₁ and IC₂ convert the reference and local-oscillator (LO) frequencies to digital signals. The 2-to-4-line demultiplexer IC₃ then samples these frequencies at 800 Hz (every 1.25 msec). The reference and LO frequencies may differ, but each must be an integral multiple of the sampling rate if the system is to achieve lock.

To set the sampling period, IC_{4A} and IC_{4B} wait for the output 110000110101 (count of 3125) from the 12-bit counter IC₅. When that output occurs, IC_{4C} issues a brief positive pulse that resets the counter and toggles the flip-flop IC₆.

Fig 3 illustrates the digital phase detection that the IC₃ demultiplexer performs. The presence of Y₁ indicates a phase lead between the LO and reference frequencies, and the duration of Y₁ indicates the

amount of phase lead. Similarly, Y₂ indicates phase lag. Y₃ goes high when both inputs are high, which ends the sample period by setting the flip-flop.

Note that in Fig 2 C₁ and C₂ convert the Y₁ and Y₂ pulses to voltage inputs for the differential amplifier IC₈. The amplifier in turn produces a dc voltage representing polarity and magnitude of the local oscillator's phase error. When locked, the loop produces narrow Y₁ and Y₂ pulses (less than 1 nsec) of equal magnitude and duration. The amplifier rejects common-mode signals such as digital noise from the demultiplexer. **EDN**

To Vote For This Design, Circle No 747

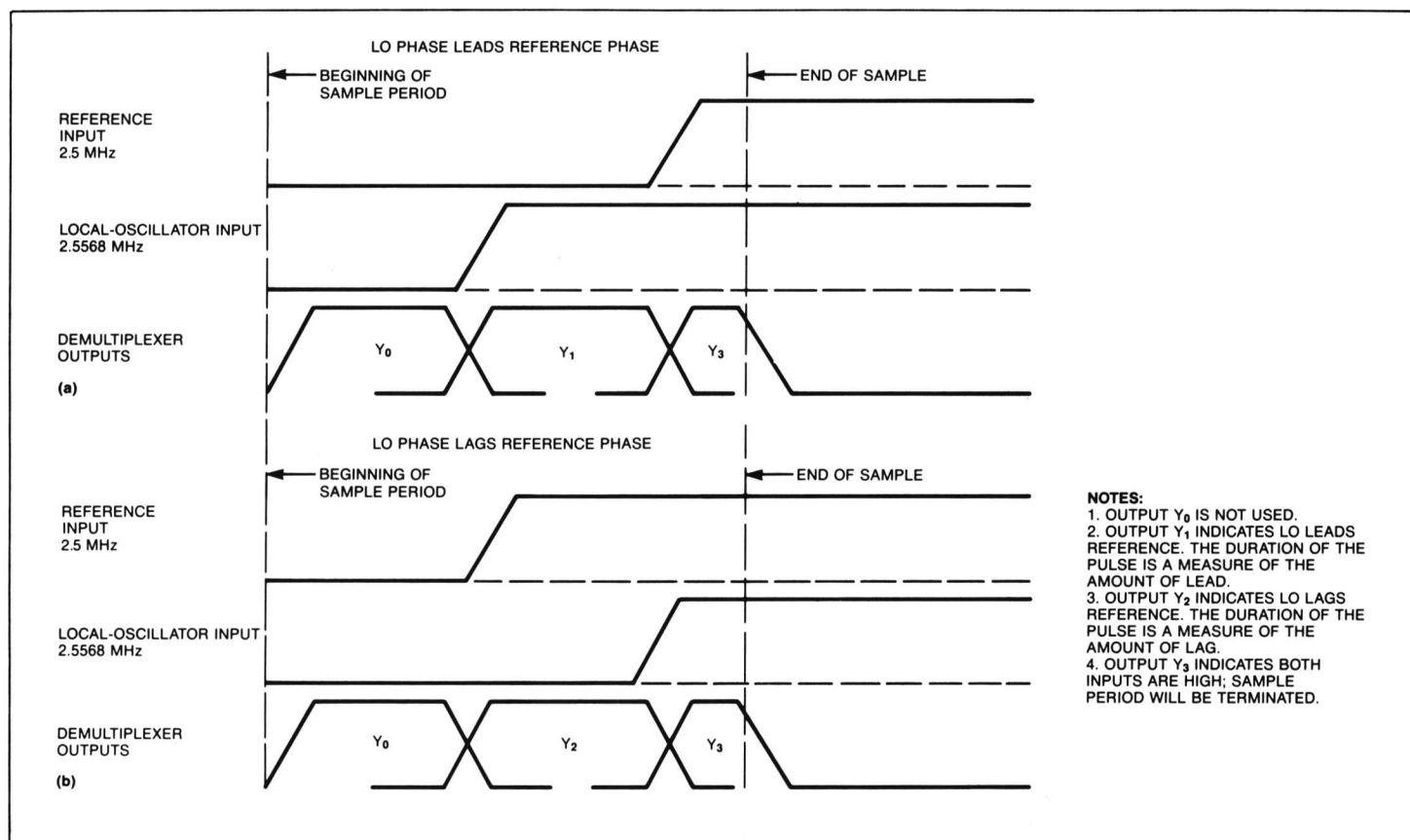


Fig 3—These waveforms depict Fig 2's operation for the cases of leading phase (a) and lagging phase (b).

Programmable integrator has 6-decade range

Mike Chang
Amber Electro Design Inc,
Montreal, Quebec, Canada

The voltage-controlled integrator of Fig 1 provides a programmable time constant for use in applications

such as programmable oscillators and programmable filters. Compared with designs based on OTAs (operational transconductance amplifiers) and monolithic multipliers, this circuit offers lower distortion, lower noise gain vs frequency, and better dynamic range. Furthermore, the circuit provides continuous remote tuning

DESIGN IDEAS

and incurs minimal noise-gain problems during tuning. A 1- to 100-kHz oscillator based on state-variable-filter topology, for example, produces -80 dB of distortion at 100 kHz and -95 dB at 1 kHz (THD plus wideband noise) where

The differential control voltage CV sets the time constant of this noninverting integrator. The resulting output is

$$V_{OUT} = \int_0^t V_{IN} dt [\log^{-1}(\log V_{IN} + V_C)],$$

$$V_C = \frac{200CV^+}{R_X + 100}.$$

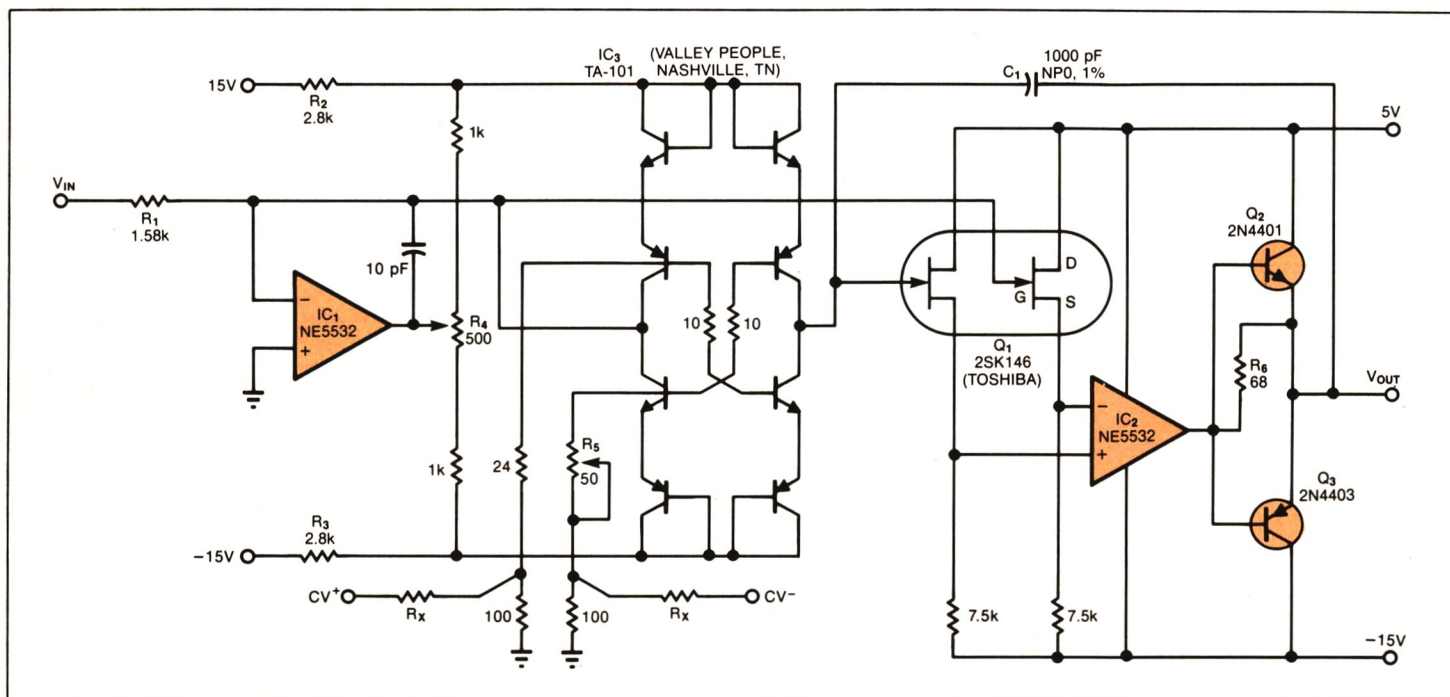


Fig 1—This noninverting integrator has a voltage-programmable time constant that you can adjust over six decades by varying the differential control voltage CV.

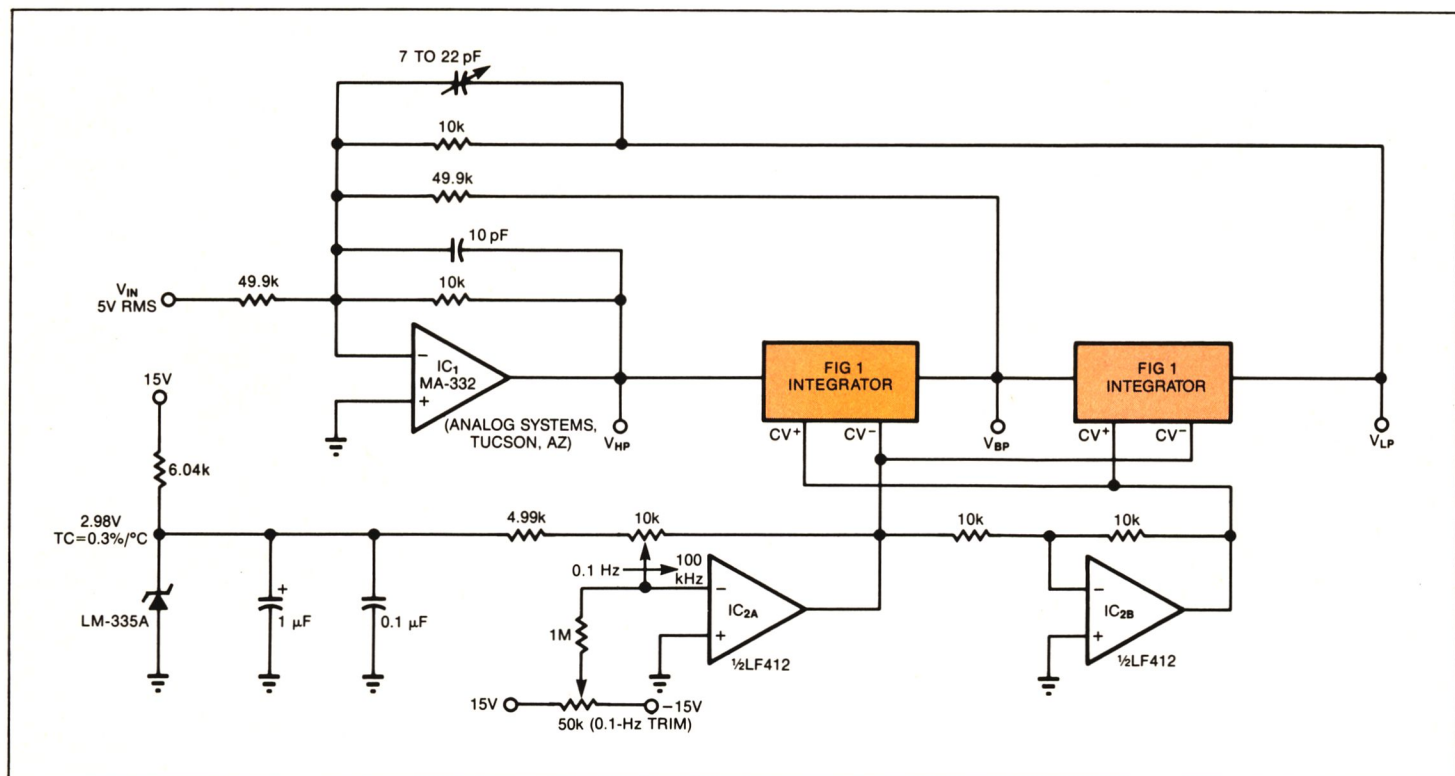


Fig 2—This 0.1- to 100-kHz filter uses two of Fig 1's integrator circuits and includes an LM-335A temperature sensor to compensate for the transistor array's 3300-ppm/°C temperature coefficient. You set the filter's cutoff frequency by adjusting the 10-k Ω potentiometer.

Design Entry Blank

\$75 Cash Award for all entries selected by editors. An additional \$100 Cash Award for winning design each issue, determined by vote of readers. Additional \$1500 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.

To: Design Ideas Editor
EDN
Cahners Publishing Co
275 Washington St, Newton, MA 02158

I hereby submit my entry for
EDN's Design Ideas program.

Name _____

Title _____ Phone _____

Company _____

Division (if any) _____

Street _____

City _____ State _____ Zip _____

Design Title _____

Home Address _____

Social Security No _____

Entry blank must accompany all entries. Design entered must be submitted exclusively to EDN, must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed _____

Date _____

Your vote determines this issue's winner. All designs published win \$75 cash. All issue winners receive an additional \$100 and become eligible for the annual \$1500 Grand Prize.

Vote now, by circling the appropriate number on the reader inquiry card.

Submit your own design, too. Mail entries to Design Ideas Editor, EDN, 275 Washington St, Newton, MA 02158.

The integrator includes an 8-transistor array connected as a complementary, cross-balanced, log-antilog multiplier. Resistors R_2 and R_3 set a 4-mA bias for the multiplier that allows low-distortion operation for inputs as high as 5V rms and 100 kHz. You trim the circuit for minimum second-harmonic distortion by adjusting R_5 at the highest operating frequency ($CV=0V$). Then, use R_4 to adjust for minimum distortion at the lowest operating frequency.

You scale the differential control voltage CV^+/CV^- by selecting R_X (two resistors) to provide the desired internal voltage range (a differential of 120 mV at the top of the 100 Ω resistors causes one decade of frequency change). $CV=0V$ produces the highest operating frequency allowed by the integrator components R_1 and C_1 , which is 100 kHz for this circuit.

The matched pair of JFET source followers (Q_1) buffers the input bias currents of op amp IC_2 and reduces output noise within the integrator's 120-dB operating range. Q_2 , Q_3 , and R_6 buffer IC_2 's output, allowing the integrator to maintain low distortion while driving capacitor C_1 and the output load.

Feedforward compensation (the connection from Q_1 to the virtual ground of IC_1) achieves a threefold increase in Q as compared to that of a simple Miller integrator. In addition, feedforward compensation counters the unwelcome Q enhancement that would otherwise occur in this circuit when used in topologies such as state-variable filters.

The transistor array exhibits a TC of 3300 ppm/ $^{\circ}C$, for which a thermistor (for example, Tel Labs' Q-81 or EQ) usually provides compensation. However, the thermistor's nonlinear TC and the difficulty of achieving tight thermal coupling between the thermistor and the array make the use of a thermistor troublesome. You can achieve more precise compensation by using an LM-335A temperature sensor as shown in Fig 2. The sensor's 2-mA bias generates the same self-heating effect as that experienced by the array. Compensation is quite effective if you protect the sensor from air currents and provide good thermal contact between the sensor and the array.

EDN

To Vote For This Design, Circle No 748