### **VERY LOW NOISE**

# OPERATIONAL -AMPLIFIER —

### BY DEREK F. BOWERS

#### **Applications**

- High Precision Instrumentation
- Microphone Preamplifier
- Tape-Head Preamplifier
- Strain-Gage Amplifier

#### **Features**

•	Very Low Voltage Noise 500pV/√ Hz
•	High Gain-Bandwidth Product 150MHz
•	High Open-Loop Gain $3 \times 10^7$
•	High CMRR 130dB
•	Very Low Offset Voltage Drift < $0.1 \mu V/^{\circ} C$


### **General Description**

In situations where low output, low-impedance transducers are used, amplifiers must have very low voltage noise to maintain a good signal-to-noise ratio. The design presented in this application note is an operational amplifier with only  $500 \, \mathrm{pV/\sqrt{Hz}}$  of broadband noise. The front end uses MAT-02 low-noise dual transistors to achieve this exceptional performance. The op amp has superb DC specifications compatible with high-precision transducer requirements, and AC specifications suitable for professional audio work.

### Principle of Operation

The design configuration in Figure 1 uses an OP-27 op amp (already a low-noise design) preceded by an amplifier consisting of three parallel-connected MAT-02 dual transistors. Base spreading resistance (R<sub>bb</sub>) generates thermal noise which is reduced by a factor of  $\sqrt{3}$  when the input transistors are parallel connected. Schottky noise, the other major noise-generating mechanism, is minimized by using a relatively high collector current (1mA per device). High current ensures a low dynamic emitter resistance, but does increase the base current and its associated current noise. Higher current noise is relatively unimportant when low-impedance transducers are used.

### Figure I Simplified Schematic

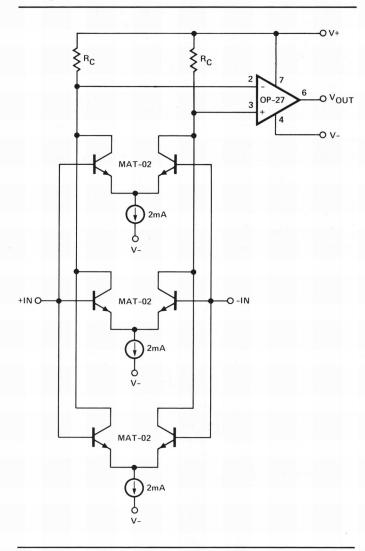

Simplified Schematic for Very-Low-Noise Operational Amplifier

## OPERATIONAL —AMPLIFIER

### VERY LOW NOISE

### Circuit Description

The detailed circuit is shown in Figure 2. A total input-stage emitter current of 6mA is provided by Q4. The transistor acts as a true current source to provide the highest possible common-mode rejection.  $R_1$ ,  $R_2$  and  $R_3$  ensure that this current splits equally among the three input pairs. The constant current in Q4 is set by using the forward voltage of a GaAsP light-emitting diode as a reference. The difference between this voltage and the base-emitter voltage of a silicon transistor is predictable and constant (to within a few percent) over the military temperature range. The voltage difference, approximately 1V, is impressed across the emitter resistor  $R_{12}$  which produces a temperature-stable emitter current.


 $R_6$  and  $C_1$  provide phase compensation for the amplifier and are sufficient to ensure stability at gains of ten and above.

 $R_7$  is an input offset trim that provides approximately  $\pm\,300\,\mu\text{V}$  trim range. The very low drift characteristics of the MAT-02 make it possible to obtain drifts of less than  $0.1\,\mu\text{V/}^\circ\text{C}$  when the offset is nulled close to zero. If this trim is not required, the  $R_4,\,R_7,$  and  $R_8$  network should be omitted and  $R_5/R_9$  connected directly to V+.

### **Amplifier Performance**

The measured performance of the op amp is summarized in Table 1. Figure 3 shows the broadband noise spectrum which is flat at about

Figure 2
Complete Amplifier Schematic

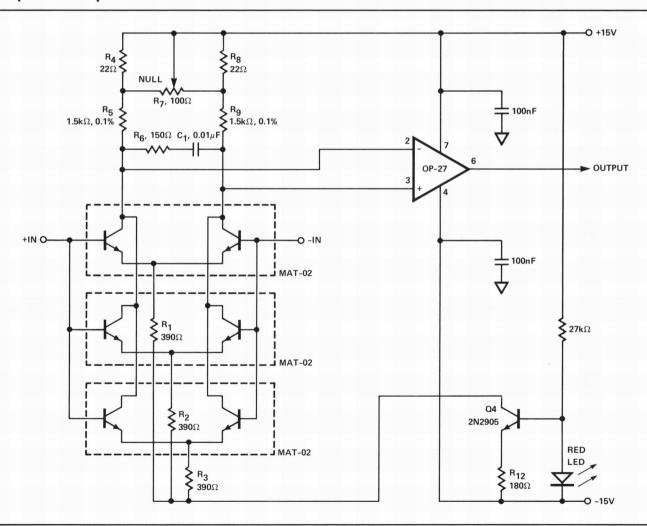

Very-Low-Noise Operational Amplifier




 $500 \text{pV}/\sqrt{\text{Hz}}$  . Figure 4 shows the low-frequency spectrum which illustrates the low 1/f noise corner at 1.5Hz. The low-frequency characteristic in the time domain from 0.1Hz to 10Hz is shown in Figure 5; peak-to-peak amplitude is less than 40nV.

### Table I Measured Performance of the Op Amp

	500pV/√ Hz
	40nV <sub>p-p</sub>
	1.5pA/√ Hz
G = 10 G = 100 G = 1000	3MHz 600kHz 150kHz
	2V/μs
	3 × 10 <sup>7</sup>
	130dB
	3μΑ
	10mA
	0.1 <sub>μ</sub> V/°C Max
G = 1000	0.002%
	G = 100 G = 1000

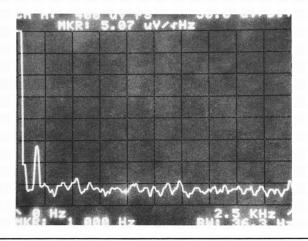
### Figure 3 Spectrum Analyzer Display Broadband



Spectrum analyzer display of broadband noise with a gain of 10,000.


Horizontal axis = 0 to 2.5kHz. Normalized vertical axis =  $830 \text{pV}/\sqrt{\text{Hz}}$  R.T.I.  $e_n = 507 pV/\sqrt{Hz}$  at 1kHz.
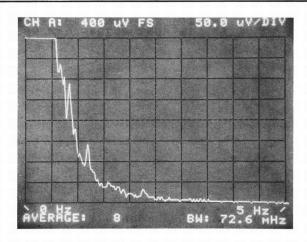
### Figure 4 Spectrum Analyzer Display Low Frequency



Low frequency noise spectrum at a gain of 10,000 showing a low 1.5Hz noise corner.

### Figure 5 Oscilloscope Display

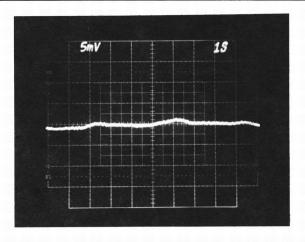

Peak-to-peak noise from 0.1 to 10Hz. Overall gain is 100,000.

### Conclusion:

Using MAT-02 matched transistor pairs operating at a high current level, it is possible to construct a high-performance, low-noise operational amplifier. The circuit uses a minimum of components and achieves performance levels impractical with monolithic amplifiers.